CBCS Scheme

USN 15CS32

Third Semester B.E. Degree Examination, June/July 2018 Analog and Digital Electronics

Time: 3 hrs. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- a. What is MOSFET? Name its types. Explain the construction of n-channel E-MOSFET.
 - b. Compare JFET and MOSFET. (05 Marks)
 - c. Explain self-bias circuit for JFET. (05 Marks)

OF

- 2 a. Define: i) CMRR ii) Slew rate iii) PSRR iv) Bandwidth pertaining to OPAMP.
 (06 Marks)
 - b. Explain with schematics operation of relaxation oscillator with relevant waveforms.

 (05 Marks)
 - c. What are active filters? Explain active low pass filter. (05 Marks)

Module-2

- 3 a. Using Q-M method, simplify the expression $f(A, B, C, D) = \Sigma(0, 3, 5, 6, 7, 11, 14)$.
 - b. Explain about positive and negative logic prove that positive 'OR' is equal to negative 'AND'.
 - c. What are Hazards? Briefly describe about designing Hazard free circuit. (05 Marks)

OR

- 4 a. Give Sum-Of-Product (SOP) and Product-Of-Sum (POS) circuit for
 - $f(A, B, C, D) = \sum m (6, 8, 9, 10, 11, 12, 13, 14, 15).$ (06 Marks) b. Explain the verilog program structure. (05 Marks)
 - c. Design a logic circuit to provide an output when any two or three of four switches are closed. (05 Marks)

Module-3

- 5 a. Implement the following Boolean function using 4:1 multiplexer $F(A, B, C, D) = \sum m (0, 1, 2, 4, 6, 9, 12, 14)$.
 - b. Construct 16:1 multiplexer using 4:1 and 2:1 multiplexer. (05 Marks)
 - Ca What is a decoder? Give the circuit for 3:8 decoder. (05 Marks)

OR

- 6 a. What is a magnitude comparator? Explain a 1-bit comparator with truth table and circuit diagram. (06 Marks)
 - b. Briefly explain about parity generators and checkers. For a 3 bit message, give the expression for even parity bit.

 (05 Marks)
 - c. Compare and contrast PLA and PAL. (05 Marks)

1 of 2

www.vturesource.com

15CS32

Module-4

- 7 a. Explain the working of JK master slave flip-flop with a sketch, truth table and symbol.
 - b. Give a brief account an flip flop as finite state machine. (06 Marks)

 (06 Marks)
 - c. Briefly describe about sequential logic circuit. (05 Marks)

OR

- 8 a. Enumerate different types of shift registers. Explain Serial In Serial Out (SISO) register.
 (06 Marks)
 - b. Mention the applicators of shift registers. (05 Marks)
 - c. Using behavioral model write verilog HDL code for a 'D' flipflop with reset input.

 (05 Marks)

Module-5

- 9 a. Explain digital clock with block diagram. (06 Marks)
 - b. Design a 3 bit synchronous binary counter using JK flip flop. (05 Marks)
 - c. Mention different types of A/D converters and test its specifications. (05 Marks)

OR

- 10 a. Explain binary weighted resistor D/A converter. Mention its drawbacks. (06 Marks)
 - b. Describe about successive approximation type ADC. (05 Marks)
 - c. What is the resolution of a 12 bit D/A converter which uses a binary ladder, if the full scale output is +10V?
 (05 Marks)

2 of 2